

Lab2: BCD 转换二进制电路的设计与实现

实验介绍

本实验通过使用 ISE 软件进行 BCD 转二进制的模块设计。

实验目标

学习 8 位 BCD 码转换二进制的转换电路实现。

实验步骤

1. 编写 8 位 BCD 码转换二进制模块的 verilog 代码。
 2. 将 8 位 BCD 转换二进制的 verilog 代码作为顶层文件生成 project。
 3. 仿真验证、综合、下载到实验板（详细过程可参考 Lab0），实现可以在 8 个发光二极管输出二进制结果的电路。
-

实验原理

1. 将开关分成两组，表示 8 位 BCD，十位 SW[7:4]，个位 SW[3:0]；
 2. 采用 8 个发光二极管 LD[7:0]作为转换后二进制的输出。
-

参考 UCF 文件

```
# Pin assignment for LEDs
NET "LD<7>" LOC = "G1" ; # Bank = 3, Signal name = LD7
NET "LD<6>" LOC = "P4" ; # Bank = 2, Signal name = LD6
NET "LD<5>" LOC = "N4" ; # Bank = 2, Signal name = LD5
NET "LD<4>" LOC = "N5" ; # Bank = 2, Signal name = LD4
NET "LD<3>" LOC = "P6" ; # Bank = 2, Signal name = LD3
NET "LD<2>" LOC = "P7" ; # Bank = 3, Signal name = LD2
NET "LD<1>" LOC = "M11" ; # Bank = 2, Signal name = LD1
NET "LD<0>" LOC = "M5" ; # Bank = 2, Signal name = LD0

# Pin assignment for SWs
NET "SW<7>" LOC = "N3"; # Bank = 2, Signal name = SW7
NET "SW<6>" LOC = "E2"; # Bank = 3, Signal name = SW6
NET "SW<5>" LOC = "F3"; # Bank = 3, Signal name = SW5
NET "SW<4>" LOC = "G3"; # Bank = 3, Signal name = SW4
NET "SW<3>" LOC = "B4"; # Bank = 3, Signal name = SW3
NET "SW<2>" LOC = "K3"; # Bank = 3, Signal name = SW2
```

NET "SW<1>" LOC = "L3"; # Bank = 3, Signal name = SW1

NET "SW<0>" LOC = "P11"; # Bank = 2, Signal name = SW0